

TRIBHUVAN UNIVERSITY
FACULTY OF MANAGEMENT

Office of the Dean

January 2021

Full Marks: 60

Pass Marks: 30

Time: 1.5 Hrs.

BIM / First Semester / IT 212: Digital Logic Design

Candidates are required to answer the questions in their own words as far as practicable.

Answer any SIX questions:

[6 × 10 = 60]

1. (a) If $A = (101)_{10}$ and $B = (11)_{10}$, then calculate $B-A$ using 2's Complement method.
(b) Convert $(1983.22)_{10}$ to octal.
2. If $F = (A+B+D)'(A+C)(A+C+D)'(A'+B+C')$ then minimize it using K-MAP and design a circuit using minimum number of NOR gates only.
3. Design 1X11 de-multiplexer using NAND gates only.
4. Design MOD 33 asynchronous counter.
5. Design Bidirectional shift register and operate it with 110111 from both ends.
6. Design a sequence recognizer that detect the sequence 1001, the machine will produce output "1" when a given sequence is detected, if not detected the output will be "0".
7. Illustrate the differences between T and D Flip-Flop along with its characteristics table, excitation table and characteristics equation.
8. Write Short Notes on :
 - a. PLA
 - b. ULSI
 - c. Memory organization
 - d. Digital Codes

